



**WEST BENGAL STATE UNIVERSITY**  
B.Sc. Honours PART-II Examinations, 2018

**ELECTRONICS-HONOURS**

**PAPER-ELTA-III-A**

Time Allotted: 2 Hours

Full Marks: 50

*The figures in the margin indicate full marks.  
Candidates should answer in their own words and adhere to the word limit as practicable.  
All symbols are of usual significance.*

**Group-A**

1. Answer any **five** questions from the following: 2×5 = 10
- (a) Define Array and Pointer in C.
  - (b) Explain the necessity of Loops in C.
  - (c) What is the difference between actual and formal arguments?
  - (d) Explain electron scattering.
  - (e) What do you mean by thermoionic work functions of a metal?
  - (f) State Bloch's theorem in one dimension.
  - (g) Show that the packing fraction for fcc lattice is  $\frac{\pi\sqrt{2}}{6}$ .
  - (h) Why are the effective mass of electron and hole different?
  - (i) How can a position be notified in stack?

**Group-B**

- Answer any **three** questions from the following 5×3 = 15
2. Write a C-program to produce the following output: 5
- ```
A B C D E D C B A
A B C D D C B A
A B C C B A
A B B A
A A
```
3. Write a C-program to find smallest and largest elements from one dimensional array elements. 5
4. Using Runge-Kutta Method write a C-program to solve the following differential equation with initial conditions  $x_0 = 0$  and  $y_0 = 1$  from  $x = 0$  to  $x = 0.4$  for an interval of  $h = 0.1$  5
- $$\frac{dy}{dx} = x + y.$$

5. (a) Define recursive function. 1  
(b) Using pointer, write a C-program to print and calculate the sum of the following series. 4
- $$S = 1^1 + 2^2 + 3^3 + \dots + 100^{100}$$
6. Write a C-program to find the roots of a quadratic equation  $ax^2 + bx + c = 0$ . 5
7. Write a program to print all Armstrong number from 1 to  $N$ . Take  $N$  as an input. 5

**Group-C**

Answer Question No. 8 and any *two* questions from the rest

8. Write a short note on any *one* of the following: 5
- (a) Concepts of Energy bands in degenerate semiconductors.
  - (b) Amorphous solids.
  - (c) Widemann-Franz Law and its validity.
9. (a) How does the potential energy of an electron vary in an infinite one dimensional crystal? 4+6  
(b) Prove that the Fermi Energy of the electron in a metal at 0 K is
- $$E_F = \frac{h^2}{8m} \left( \frac{3n}{\pi} \right)^{\frac{2}{3}}, \text{ where } h = \text{Planck's constant}$$
- $m = \text{mass of an electron}$   
 $n = \text{electron concentration}$
- 10.(a) What are the assumptions of Drude-Lorentz model to explain classical free electron theory of metals? Discuss the achievements and failures of this model. (3+4)+3  
(b) What happens to the Hall voltage if thickness of the specimen is doubled? Justify your answer.
- 11.(a) Distinguish between a metal, semiconductor and insulator using their band-diagram. 5+(3+2)  
(b) Explain the concept of Brillouin zone with suitable diagram.
- 12.(a) Differentiate between direct and indirect band-gap semiconductors with examples. 3+4+3  
(b) Derive expression for the electron and hole concentration of an intrinsic semiconductor.  
(c) How does Fermi level shift with increasing doping and increasing temperature in an extrinsic semiconductor.



**WEST BENGAL STATE UNIVERSITY**

B.Sc. Honours PART-II Examinations, 2018

**ELECTRONICS-HONOURS**

**PAPER-ELTA-IV**

Time Allotted: 4 Hours

Full Marks: 100

*The figures in the margin indicate full marks.  
Candidates should answer in their own words and adhere to the word limit as practicable.*

**Group-A**


**[Active Device]**

**(Marks-25)**

**Answer Question No. 1 and any two questions from the rest**

1. Answer any *five* questions from the following: 1×5 = 5
  - (a) How does the width of a  $p-n$  junction depletion region vary with impurity concentration?
  - (b) Why is the common collector mode also called emitter follower?
  - (c) In the CB mode  $I_C < I_E$ , although BJT acts an amplifier – Explain.
  - (d) Why is an  $n$ -channel FET preferred over a  $p$ -channel FET?
  - (e) Define reverse saturation current.
  - (f) What do you mean by thermal runaway?
  - (g) Define firing angle of an SCR.
  - (h) Why is a JFET, known as a square-law device?
  
2. (a) Draw the circuit diagram of a full-wave rectifier and explain its working principle. Find out the ripple factor and conversion efficiency of this rectifier. 1+2+2+2
  - (b) Explain how a Zener-diode can act as a voltage regulator. 3
  
3. Starting from Poisson's equation, derive expressions for (a) contact potential, (b) depletion width and (c) junction capacitance of a  $p-n$  junction diode. 3+3.5+3.5
  
4. (a) Explain that I-V characteristics of an SCR using two-transistor analogy. 6
  - (b) What is meant by pinch-off in a JFET? Explain why complete pinch-off cannot occur. 4

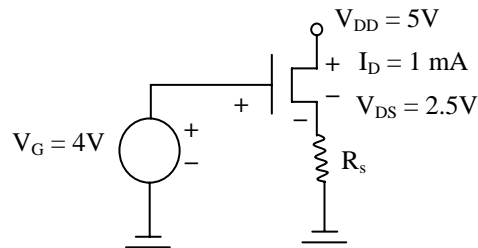5. (a) With suitable diagrams explain the operation of a MOSFET, as a voltage variable resistor. – Explain how the JFET can be used as an automatic gain control device. 4+2
- (b) For the circuit shown below use the NMOS equation to find  $R_S$  &  $K$ . Mention the region of operation. Consider  $V_T = 1\text{ V}$  3+1



### Group-B

#### [Active Circuits]

(Marks-40)

Answer Question No. 6 and any *three* questions from the rest

6. Answer any *five* questions from the following: 2×5 = 10
- Define  $\alpha$  and  $\beta$  in connection with a transistor.
  - What is cross over distortion?
  - How is a power transistor different from a normal transistor?
  - Define gain margin of an amplifier.
  - What is TUF?
  - Can the stability factor be less than unity? – Explain.
  - State the advantages of SMPS over linear power supply.
  - Why is a push-pull amplifier so called?
7. With the help of necessary diagram, explain the working principle of phase-shift oscillator. Derive the expressions for frequency of oscillation and condition of sustained oscillation. 2+3+3+2
8. (a) What is harmonic distortion? How does push-pull amplifier minimize harmonic distortion? 3+4
- (b) The open-loop gain of an amplifier changes by 25% due to changes in the parameters of the device. If a maximum change of 4% in overall gain, what should be the type of feedback employed? If the gain with feedback is 20. Find the minimum value of feedback ratio and open-loop gain. 3
9. (a) State and prove Miller's theorem and write down the dual of it. 3+1
- (b) Draw the schematic block diagram of an SMPS and explain the function of each block. 6

- 10.(a) Define the following terms and find an inter-relationship between them: 3+2
- (i) trans-conductance
  - (ii) drain resistance
  - (iii) amplification factor.
- (b) An  $n$ -channel JFET has  $I_{DSS} = 10$  mA and pinch-off voltage  $V_P = -4$  V. Find the drain current for  $V_{GS} = -2$  V. If the transconductance  $g_m$  of the JFET with the same  $I_{DSS}$  at  $V_{GS} = 0$  V is 4 millimho, find the pinch-off voltage. 5
- 11.(a) What are the advantages of negative feedback? Show how negative feedback (i) stabilizes gain, (ii) improves input impedance of an amplifier. 3+2+3
- (b) Show that the CE configuration introduces a  $180^\circ$  shift in the output. 2

**Group-C**


**[Instrumentation]**

**(Marks-35)**

**Answer Question No. 12 and any *three* questions from the rest**

12. Answer any *five* questions from the following: 1×5 = 5
- (a) What is the slew rate of an OPAMP?
  - (b) Define virtual ground of an OPAMP.
  - (c) What is meant by passive and active probe?
  - (d) What is the persistence of phosphor?
  - (e) State two disadvantages of closed loop system.
  - (f) Define capture range in connection with a V.C.O.
  - (g) What is the function of delay line in CRO?
- 13.(a) Draw the block diagram of a general purpose CRO and explain the functions of the following controls: 2+5
- (i) Intensity
  - (ii) Focus
  - (iii) Horizontal and vertical positioning
  - (iv) Synchronization.
- (b) Explain the various types of coupling used in CRO. 3
- 14.(a) Draw the circuit diagram of a monostable multivibrator using 555 timer I.C and obtain the expression for its time period and duty cycle. 7
- (b) Draw the circuit and explain the operation of a time-base circuit. 3

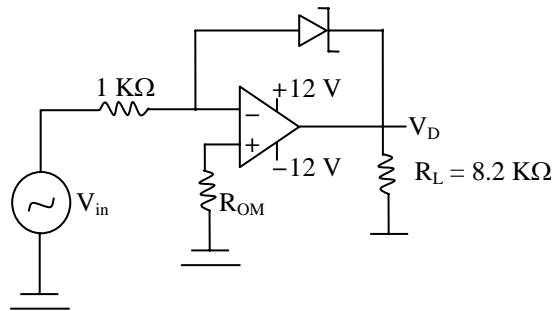- 15.(a) Determine the output voltage swing and draw the output waveform of the given circuit, if a sine wave of frequency 100 Hz and amplitude 1V is applied at its input. Assume that  $V_D = 0.7V$  and  $V_Z = 4.7V$ . 5



- (b) Write a short note on V.C.O. 5
- 16.(a) Draw a block diagram of the various steps of an OPAMP. 4+3+3
- (b) What is the function of level shifter?
- (c) Find expression for input impedance of an inverting amplifier.