



WEST BENGAL STATE UNIVERSITY
B.Sc. Honours 4th Semester Examination, 2022

ELSACOR09T-ELECTRONICS (CC9)

Time Allotted: 2 Hours

Full Marks: 40

*The figures in the margin indicate full marks.
Candidates should answer in their own words and adhere to the word limit as practicable.
All symbols are of usual significance.*

GROUP-A

1. Answer any **five** questions from the following: 2×5 = 10
- (a) What are even signals? Give examples.
 - (b) Write down the difference between energy and power signals.
 - (c) Find the fundamental period of $x(n) = \sin 2\pi n + \exp(j7\pi n/3)$.
 - (d) What is the relation between impulse and unit step signals?
 - (e) State Dirichlet's conditions for a function to be expanded as a Fourier series.
 - (f) State the Final value theorem of Laplace Transform.
 - (g) Clearly explain periodic signal.
 - (h) Explain the function of memory element in LTI system.

GROUP-B

Answer any six questions from the following

5×6 = 30

2. State and prove Parseval's theorem for power signal. 1+4
3. (a) Derive the Laplace transform of the function $x(t) = e^{-2t} \sin 4\pi t$. 3
- (b) Given, $x(n) = \alpha^n$ for $n \geq 0$ and 0 for $n < 0$. Show that for $\alpha < 1$, $x(n)$ is an energy signal. 2
4. Derive the unit ramp response of a second order unity feedback system in time domain. Hence, find the lagging time and the time constant of the system. 3+1+1
- Given Transfer function $G(S) = \frac{K}{S(1+ST)}$.

5. A square pulse of amplitude 3 volt is defined as: 3+2

$$x(t) = 3 \text{ for } 0 \leq t < 4$$

$$= 0 \text{ for } 4 \leq t \leq \infty.$$

$x(t)$ is applied to a series R-C circuit of capacitance. $1 \mu\text{F}$ and resistance $1 \text{ k}\Omega$. Consider the output is obtained across resistance and the capacitor is initially uncharged. Hence, derive the unit impulse response in S domain and find the output voltage at $t = 1.5 \text{ sec}$.

6. (a) Apply the symmetry property of Fourier transform, show that $2\frac{1}{2}$
 $\delta(t+T) - \delta(t-T) = 2j \sin Tw$.

- (b) Show that the Fourier transform of a Gaussian pulse is also Gaussian in nature. $2\frac{1}{2}$

7. (a) Find the convolution integral of $x(t)$ and $h(t)$. Given that,

$$x(t) = 1, 0 \leq t \leq 2a;$$

$$h(t) = \delta(t+2a) - \delta(t-2a);$$

Draw the final diagram after convolution.

- (b) Find the result of the convolution of $x(-t) * \delta(-t-t_0)$.


8. Express $f(x) = \frac{1}{2}(\pi - x)$ as a Fourier series with period 2π to be valid in the 5
interval 0 to 2π . Hence, deduce the value of the series $1 - \frac{1}{3} + \frac{1}{5} - \frac{1}{7} + \dots$

9. Show that, a linear system can be completely characterized by its impulse response. 5

- 10.(a) Determine whether the discrete time LTI system with impulse response 2+1
 $h(n) = (.9)^n u(n-1)$ is BIBO stable or not. Is it causal?

- (b) Define stability of a LTI system. 2

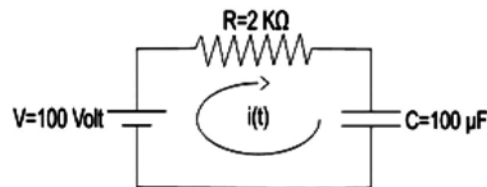11. For circuit below, calculate the initial charging current of capacitor using Laplace Transform. 5



N.B. : Students have to complete submission of their Answer Scripts through E-mail / Whatsapp to their own respective colleges on the same day / date of examination within 1 hour after end of exam. University / College authorities will not be held responsible for wrong submission (at in proper address). Students are strongly advised not to submit multiple copies of the same answer script.

—x—



WEST BENGAL STATE UNIVERSITY

B.Sc. Honours 4th Semester Examination, 2022

ELSACOR08T-ELECTRONICS (CC8)

Time Allotted: 2 Hours

Full Marks: 40

*The figures in the margin indicate full marks.
Candidates should answer in their own words and adhere to the word limit as practicable.
All symbols are of usual significance.*


GROUP-A

1. Answer any **five** questions from the following: 2×5 = 10
 - (a) What is the cause of slow rate in an OP-AMP? 2
 - (b) How does CMRR of OP-AMP vary with frequency? 2
 - (c) What is the utility of an unity-gain buffer? 2
 - (d) Why are dual power supply voltages provided to an OP-AMP? 2
 - (e) Find input impedance of inverting amplifier using OP-AMP. 2
 - (f) Why is a stable multivibrator called as free running multivibrator? 2
 - (g) Write down the significance of zero output impedance of an ideal OP-AMP. 2
 - (h) State any two factors responsible for offset voltage in an OP-AMP. 2

GROUP-B


Answer any six questions from the following 5×6 = 30

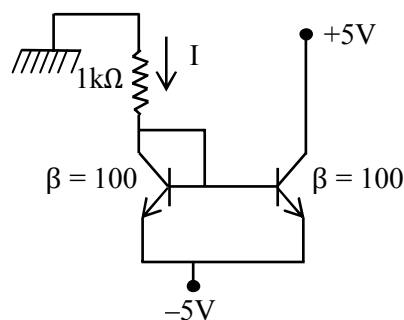2. Derive the condition of oscillation in a Wien-bridge oscillator. Hence explain how amplitude stabilization is achieved in an OP-AMP based implementation of the oscillator. 3+2
3. Realise a bistable multivibrator using IC 555 and explain its operation. 2+3
4. (a) Show that the circuit functions as a current mirror and find the value of I. 4




- (b) Define PSRR of an OP-AMP. 1
5. (a) Find expression for the gain of a non-inverting amplifier assuming the gain to be finite. 3

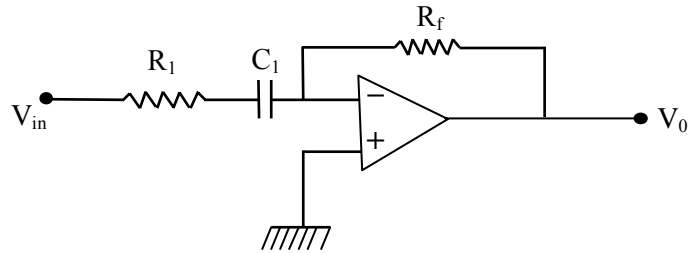- (b) Explain with reason, the type of filter realized by the given circuit. 2



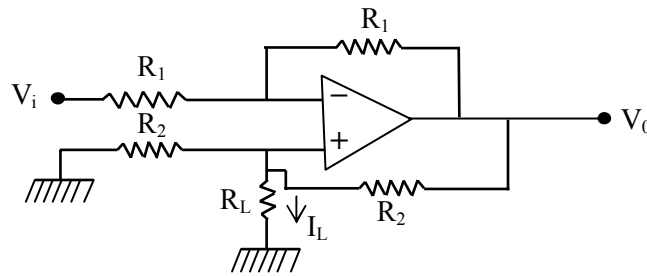6. (a) Find the value of I_L in the given circuit. 3



- (b) What are the unique characteristics of differential amplifier? 2
7. Describe how an OP-AMP can be used as a square-wave generator and find out the expression of frequency of the output. 5
8. (a) Explain with a block diagram, how OP-AMPs can be used for multiplication of two voltages. 3
 (b) Draw and explain the transfer characteristics of an OP-AMP. 2
9. (a) Find expression for output voltage of a practical integrator. 3
 (b) What are the advantages of active filter over passive filter? 2
- 10.(a) For a similar gain, explain the advantage of non-inverting mode over non-inverting mode of operation. 2
 (b) Draw a labelled block diagram of the different stages of an OP-AMP and explain the function of each stage. 3
- 11.(a) Design a practical integrator that integrates signals with frequency down to 500 Hz. It produces a peak output of 0.5 V when the input is a sine wave with a peak amplitude of 10 V with a frequency of 10 kHz. 3
 (b) Design an active first order low pass butterworth filter with cut-off frequency 1 kHz and for a given gain 3.2 (Given $C = 0.1 \mu\text{F}$). 2

N.B. : Students have to complete submission of their Answer Scripts through E-mail / Whatsapp to their own respective colleges on the same day / date of examination within 1 hour after end of exam. University / College authorities will not be held responsible for wrong submission (at in proper address). Students are strongly advised not to submit multiple copies of the same answer script.

—x—